

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY-GURAJADA VIZINAGARAM
II B. Tech I Semester Regular/Supply Examinations, November – 2025
ELECTRONIC DEVICES AND CIRCUITS
(ECE)

Time: 3 hours**Max. Marks: 70***Question paper consists of Part A, Part B.**Part A is compulsory, Answer all questions.**In Part B, Answer any one question from each unit.***PART-A****(20 Marks)**

- 1 a) Define depletion region in a PN junction. [2]
- b) Write the equation for diode current and explain its terms. [2]
- c) What is the Early effect? [2]
- d) List the advantages of a transistor as a switch. [2]
- e) Write two differences between JFET and MOSFET. [2]
- f) What is pinch-off voltage? [2]
- g) What are stability factors? [2]
- h) Define thermal runaway. [2]
- i) Write the main features of a CE amplifier. [2]
- j) Define hybrid- π model. [2]

PART-B**(50 Marks)****Unit-1**

- 2 a) Demonstrate the construction and working of a PN junction diode with energy band diagrams. [5]
- b) Explain the construction and working of LED, LCD, and photodiode. [5]

(OR)

- 3 a) Demonstrate the operation full-wave rectifier with filters for waveform. [5]
- b) Discuss different breakdown mechanisms in a diode with neat diagrams. [5]

Unit-2

- 4 a) Describe the input and output characteristics of CB, CE, and CC configurations. [5]
- b) Explain the operation and characteristics of a phototransistor. [5]

(OR)

- 5 a) Describe the working of a transistor as a switch and list the switching times. [5]
- b) Explain the Ebers-Moll model of a transistor. [5]

Unit-3

- 6 a) Demonstrate the construction, operation, and characteristics of a JFET. [5]
- b) Explain the construction and working of depletion and enhancement-type MOSFETs. [5]

(OR)

- 7 a) Compare BJT and JFET in terms of operation and characteristics. [5]
- b) Describe the operation of CMOS and Bi-CMOS inverter circuits. [5]

Unit-4

- 8 a) Demonstrate FET biasing methods and their stabilization. [5]
- b) Discuss about the need for biasing in detail. [5]

(OR)

- 9 a) Derive the expression for stability factors S , S' , and S'' . [5]
- b) Discuss bias compensation techniques using diodes and thermistors. [5]

Unit-5

- 10 a) Explain the h-parameter model and analyze a CE amplifier using it. [5]
- b) Derive voltage gain and input/output impedance for CB and CC amplifiers. [5]

(OR)

- 11 a) Compare BJT amplifier configurations based on gain and impedance. [5]
- b) Illustrate the small-signal model of a FET and analyze CS, CG, and CD amplifiers. [5]

